

CONTROL SYTEMS

TOPIC TWO

TRANSFER FUNCTION

Transfer Function plays an important role in the characterization of Linear Time-invariant Systems.

The starting point of defining the Transfer Function is the Differential equation

A transfer function between an input variable & an output variable of a system is defined as the ratio of the Laplace Transform of the Output to the Laplace Transform of the Input

Transfer Function is defined only for a Linear System & strictly only for Time-invariant Systems


All initial conditions of the system are assumed to be zero.

A Transfer Function is independent of the Input excitation

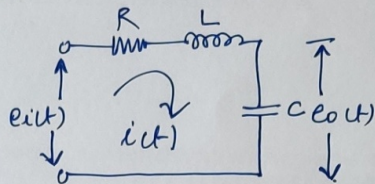Example

① The following example illustrates how transfer function for a linear system can be derived.

② A series RLC circuit is shown in Fig below



③ The input variable is designated by $e_i(t)$

④ The output variable is the current $i(t)$

⑤ The loop equation of the network is

$$E_i(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

⑥ Taking Laplace transform on both sides and assuming zero initial conditions,

$$E_i(s) = R I(s) + s L I(s) + \frac{1}{Cs} I(s)$$

$$= \left[R + sL + \frac{1}{Cs} \right] I(s)$$


$$\frac{I(s)}{E_i(s)} = \frac{1}{R + sL + \frac{1}{Cs}} = \frac{Cs}{Ls^2 + RCs + 1}$$

⑦ If the voltage across the capacitor $e_o(t)$ is considered as an output, the transfer function between $e_i(t)$ and $e_o(t)$ is obtained as

$$\begin{aligned} E_o(s) &= \frac{1}{Cs} I(s) \\ &= \frac{1}{Cs} \cdot \frac{Cs}{Ls^2 + RCs + 1} E_i(s) \end{aligned}$$

$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{1}{Ls^2 + RCs + 1}}$$

Transfer function of RC network

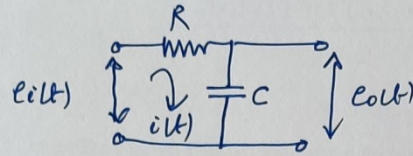

$$e_i(t) = Ri(t) + \frac{1}{C} \int i(t) dt$$

$$E_i(s) = RI(s) + \frac{1}{Cs} I(s)$$

$$E_o(s) = \left[R + \frac{1}{Cs} \right] I(s) = \left[\frac{R(s+1)}{Cs} \right] I(s)$$

$$e_o(t) = \frac{1}{C} \int i(t) dt$$


$$= \frac{1}{Cs} I(s)$$


$$= \frac{1}{Cs} \cdot C \cdot \frac{E_i(s)}{R(s+1)}$$

$$\boxed{\frac{E_o(s)}{E_i(s)} = \frac{1}{R(s+1)}}$$

Pb For the circuit given in Fig below, if $C = 1 \mu F$, what values of R_1 and R_2 will give $T = 0.6 \text{ sec}$ and $a = 0.1$. The expression for transfer function is
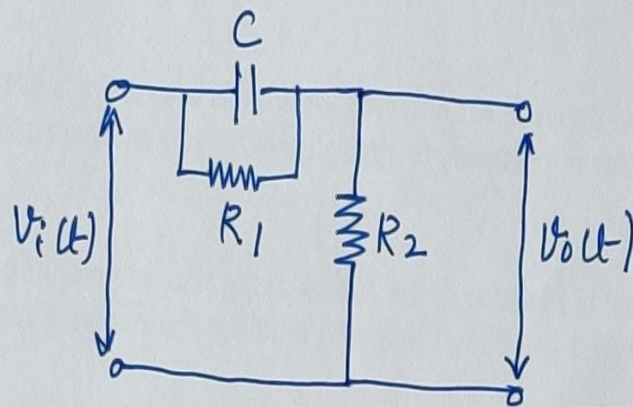
$$\frac{V_o(s)}{V_i(s)} = \frac{a(1+sT)}{1+a sT}$$



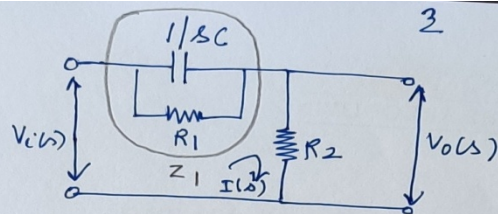

$$Z_1(s) = \frac{R_1 \cdot \frac{1}{sC}}{R_1 + \frac{1}{sC}} = \frac{R_1}{R_1Cs + 1}$$

$$V_i(s) = \left[\left(\frac{R_1}{R_1Cs + 1} \right) + R_2 \right] I(s) \longrightarrow \textcircled{1}$$

$$V_o(s) = R_2 I(s)$$

$$\therefore V_o(s) = R_2 \left[\frac{V_i(s)}{\frac{R_1}{R_1Cs + 1} + R_2} \right] \longrightarrow \text{From } \textcircled{1}$$

$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{R_2 (R_1Cs + 1)}{R_1 + R_2 (R_1Cs + 1)} \\ &= \frac{R_2 C R_1 Cs + 1}{R_1 + R_2 R_1 Cs + R_2} \\ &= \frac{R_2 C R_1 Cs + 1}{(R_1 + R_2) \left(1 + \frac{R_1 R_2 Cs}{R_1 + R_2} \right)} \\ &= \frac{\left(\frac{R_2}{R_1 + R_2} \right) (1 + R_1Cs)}{\left[1 + \left(\frac{R_1 R_2}{R_1 + R_2} \right) Cs \right]} \\ &= \frac{a (1 + sT)}{1 + aTs} \end{aligned}$$

Comparing with given equation

$$a = \frac{R_2}{R_1 + R_2}, \quad T = R_1 C$$

$$T = 0.6 \text{ sec}, \quad C = 1 \mu\text{f}$$

$$R_1 = \frac{0.6}{10^{-6}} = 600 \text{ k}$$


$$\boxed{R_1 = 600 \text{ k}}$$

$$a = 0.1 = \frac{R_2}{R_1 + R_2}$$

$$= \frac{R_2}{600 \text{ k} + R_2}$$

$$\boxed{R_2 = 66.67 \text{ k}}$$


Pb

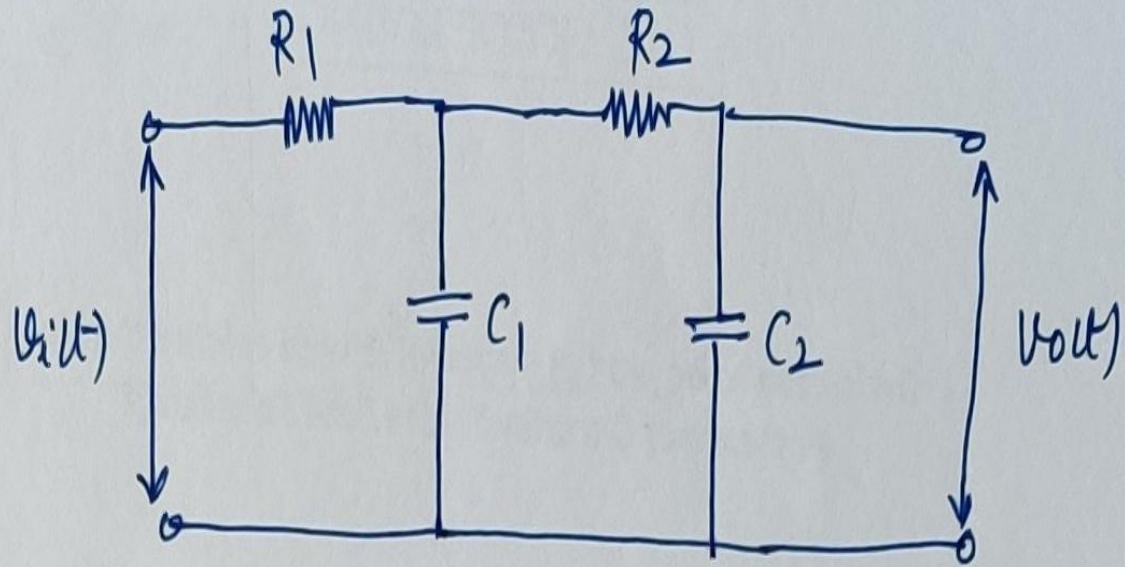

Find $\frac{v_o(s)}{v_i(s)}$

Pb2

SOLUTION

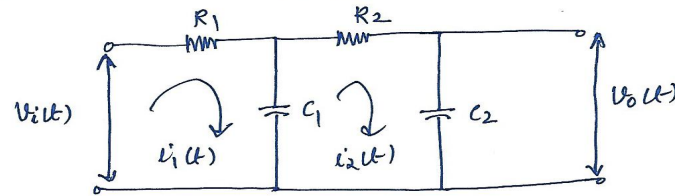

→ Writing Mesh equations

$$V_i = R_1 i_1 + \frac{1}{C_1} \int i_1 dt - \frac{1}{C_1} \int i_2 dt \rightarrow (1)$$

$$0 = -R_2 i_2 - \frac{1}{C_2} \int i_2 dt - \frac{1}{C_1} \int i_2 dt + \frac{1}{C_1} \int i_1 dt \rightarrow (2)$$

→ Taking Laplace Transforms

$$V_i(s) = R_1 I_1(s) + \frac{1}{C_1 s} I_1(s) - \frac{1}{C_1 s} I_2(s) \rightarrow (3)$$

$$0 = -R_2 I_2(s) - \frac{1}{C_2 s} I_2(s) - \frac{1}{C_1 s} I_2(s) + \frac{1}{C_1 s} I_1(s) \rightarrow (4)$$

→ Combining terms in $I_1(s)$ and $I_2(s)$

$$V_i(s) = I_1(s) \left[R_1 + \frac{1}{C_1 s} \right] - I_2(s) \frac{1}{C_1 s} \rightarrow (5)$$

$$0 = -I_1(s) \frac{1}{C_1 s} + I_2(s) \left[R_2 + \frac{1}{C_2 s} + \frac{1}{C_1 s} \right] \rightarrow (6)$$

→ Using Cramer's Rule,

$$I_2(s) = \frac{\begin{vmatrix} R_1 + \frac{1}{C_1 s} & +V_i(s) \\ -\frac{1}{C_1 s} & 0 \end{vmatrix}}{\begin{vmatrix} R_1 + \frac{1}{C_1 s} & -\frac{1}{C_1 s} \\ -\frac{1}{C_1 s} & R_2 + \frac{1}{C_2 s} + \frac{1}{C_1 s} \end{vmatrix}}$$

$$I_{2(s)} = \frac{V_{i(s)} \frac{1}{C_1 s}}{\left(R_1 + \frac{1}{C_1 s}\right) \left(R_2 + \frac{1}{C_1 s} + \frac{1}{C_2 s}\right) - \frac{1}{C_1^2 s^2}}$$

$$V_{0(s)} = \frac{1}{C_2 s} I_{2(s)} \longrightarrow (7)$$

$$V_{0(s)} = \frac{\frac{1}{C_2 s} \cdot \frac{1}{C_1 s} V_{i(s)}}{\left(R_1 + \frac{1}{C_1 s}\right) \left(R_2 + \frac{1}{C_1 s} + \frac{1}{C_2 s}\right) - \frac{1}{C_1^2 s^2}}$$

$$\frac{V_{0(s)}}{V_{i(s)}} = \frac{\frac{1}{C_1 C_2 s^2}}{\frac{(R_1 C_1 s + 1)}{C_1 s} + \frac{(R_2 C_1 C_2 s^2 + C_2 s + C_1 s)}{C_1 C_2 s^2} - \frac{1}{C_1^2 s^2}}$$

$$\begin{aligned} \frac{V_{0(s)}}{V_{i(s)}} &= \frac{\frac{1}{C_1 C_2 s^2}}{\frac{1}{C_1^2 s^2} \left[\frac{(R_1 C_1 s + 1)(R_2 C_1 C_2 s^2 + C_2 s + C_1 s)}{C_2 s} - 1 \right]} \\ &= \frac{\frac{1}{C_1 C_2 s^2}}{\frac{1}{C_1^2 s^2} \left[\frac{(R_1 C_1 s + 1)(R_2 C_1 C_2 s^2 + C_2 s + C_1 s) - C_2 s}{C_2 s} \right]} \end{aligned}$$


$$\frac{V_{o(s)}}{V_{i(s)}} = \frac{C_1 s}{(R_1 C_1 s + 1)(R_2 C_1 C_2 s^2 + C_1 s + C_2 s) - C_2 s}$$

$$\frac{V_{o(s)}}{V_{i(s)}} = \frac{C_1 s}{[R_1 C_1 s \cdot R_2 C_1 C_2 s^2 + R_1 C_1 s \cdot C_1 s + R_1 C_1 s \cdot C_2 s + R_2 C_1 C_2 s^2 + C_1 s + C_2 s - C_2 s]}$$


$$= \frac{\cancel{C_1 s} C_1 s}{C_1 s [R_1 R_2 C_1 C_2 s^2 + R_1 C_1 s + R_1 C_2 s + R_2 C_2 s + 1]}$$

$$\frac{V_{o(s)}}{V_{i(s)}} = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1}$$

Pb

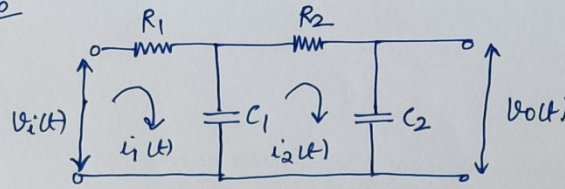

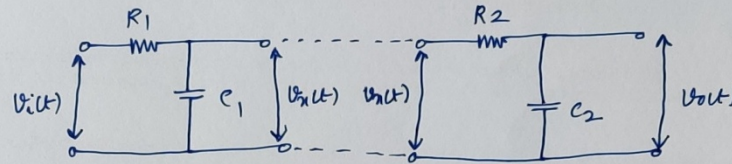Ans $\frac{V_o(s)}{V_i(s)} = \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_2 C_2) s + 1}$



$$\frac{V_1(s)}{V_i(s)} = \frac{1}{R_1 C_1 s + 1}, \quad \frac{V_o(s)}{V_3(s)} = \frac{1}{R_2 C_2 s + 1}$$

$$\frac{V_2(s)}{V_i(s)} \times \frac{V_o(s)}{V_3(s)} = \frac{1}{(R_1 C_1 s + 1)} \times \frac{1}{(R_2 C_2 s + 1)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{(R_1 C_1 s + 1) (R_2 C_2 s + 1)}$$

$$= \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_2 C_2) s + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_2 C_2) s + 1}$$

IMPULSE RESPONSE


- For a Linear Time-Invariant System , the transfer function $T(s)$ is the ratio of $C(s)$ / $R(s)$, where $R(s)$ & $C(s)$ are the Laplace transforms of the Input & Output respectively.

$$\text{Therefore, } C(s) = T(s) R(s)$$

- Consider the Output response of a system to a **Unit Impulse Input**, where initial conditions are zero.
- Since the Laplace transform of the Unit impulse function is Unity, the Laplace transform of the Output of the system is just $C(S) = T(S)$.
- The Impulse Response of a system is thus the response of a Linear system to a Unit Impulse Input ,when the initial conditions are zero.
- Thus the transfer function & the Impulse response of a LTI system , contain the same information about the system performance.
- Hence it is possible to obtain complete information about the system by exciting it with an Impulse input & measuring the response.
- In practice a pulse input with a very short duration compared with the significant time constants of the system can be used.

BLOCK DIAGRAMS

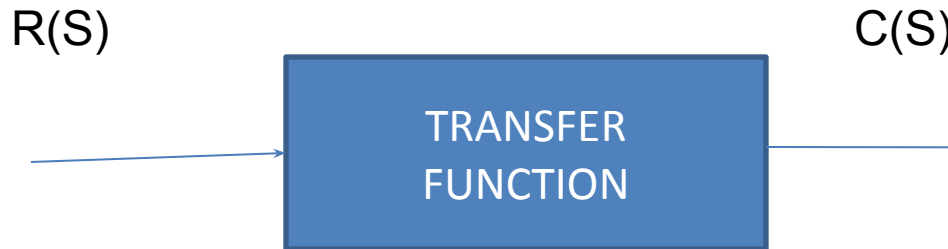- A block diagram of a system is a pictorial representation of the functions performed by each component & of the flow of signals.
- The transfer function of the components are usually entered in the corresponding blocks , which are connected by arrows to indicate the direction of the flow of signals.
- Fig below shows an element of the block diagram



- The output signal is the input signal multiplied by the transfer function in the block.
- The **Error Detector or Summing Point** produces a signal which is the difference between the Reference Input & the Feedback Signal of the control system.
- A circle with a cross is the symbol which indicates a Summing operation
- The plus or minus sign at the arrow head indicates whether that signal is to be added or subtracted.

BLOCK DIAGRAMS CONT-----

- The quantities being added or subtracted should have the same dimension & same units.

