

19-11-2020

## EWE - Tutorial 4

Vedant Milind Athavale  
181090071  
TY Btech EXTC

$$Q1.] \quad a.) \quad \frac{R}{L} = \frac{G}{C} \Rightarrow G = \frac{R}{L} C = \frac{20 \times 63 \times 10^{-12}}{0.3 \times 10^{-6}}$$

$$G = 4.2 \times 10^{-3} \text{ S/m}$$

$$\alpha = \sqrt{RG} = \sqrt{20 \times 4.2 \times 10^{-3}} = 0.2898$$

$$\beta = \omega \sqrt{LC} = 2\pi \times 120 \times 10^6 \sqrt{0.3 \times 10^{-6} \times 63 \times 10^{-12}} = 3.278$$

$$\underline{\underline{\gamma = 0.2898 + j3.278 \text{ /m}}}$$

b.) Let  $V_0$  be its original magnitude

$$V_0 e^{-\alpha z} = 0.2 V_0$$

$$\Rightarrow e^{-\alpha z} = 0.2$$

$$\therefore z = \frac{1}{\alpha} \ln 5 = \underline{\underline{5.554 \text{ m}}}$$

$$c.) \quad \beta l = 45^\circ = \pi/4 \Rightarrow l = \frac{\pi}{4\beta} = \frac{4}{4 \times 3.278}$$

$$\Rightarrow \boxed{l = 0.2396 \text{ m}}$$

Q2.] We are given that there's a  $60 \Omega$  lossless line connected to a source with

$$V_g = 10 \angle 0^\circ \text{ V}_{\text{rms}} \quad \& \quad Z_g = 50 - j40 \Omega$$

Load is of  $j40 \Omega$ .

$$\text{length, } l = 100 \text{ m, } \beta = 0.25 \text{ rad/m}$$

$$a.) \quad \beta l = \frac{1}{4} \times 100 = 25 \text{ rad} = 1432.4^\circ = 352.4^\circ$$

$$Z_{\text{in}} = 60 \left[ \frac{j40 + j60 \tan 352.4^\circ}{60 - 40 \tan 352.4^\circ} \right] = \underline{\underline{j29.375 \Omega}}$$

$$V(z=0) = V_0 = \frac{Z_{in}}{Z_{in} + Z_g} V_g = \frac{j29.375 (10 \angle 0^\circ)}{j29.375 + 50 - j40}$$

$$= \frac{29.375 \angle 90^\circ}{51.116 \angle -12^\circ} = \underline{\underline{0.575 \angle 102^\circ}}$$

b.)  $Z_{in} = Z_L = j40 \Omega$

$$V_L = V_s(z=l), \quad V_0 = V_L \cdot e^{j\beta l}$$

$$V_L = V_0 \cdot e^{-j\beta l} = (0.575 \cdot e^{j102^\circ}) (e^{-j352.4^\circ})$$

$$= \underline{\underline{0.575 \angle -250.4^\circ}}$$

c.)  $\beta l = \frac{1}{4} \times 4 = 1 \text{ rad} = 57.3^\circ$

$$Z_{in} = 60 \left[ \frac{j40 + j60 \tan 57.3^\circ}{60 - 40 \tan 57.3^\circ} \right] = \underline{\underline{-j3487.11 \Omega}}$$

$$V = V_L e^{j\beta l} = (0.575 \angle -250.4^\circ) e^{j57.3^\circ}$$

$$= \underline{\underline{0.575 \angle -193.1^\circ}}$$

d.) 3 m from the source is the same as 97 m from the load, i.e.,

$$l = 100 - 3 = 97 \text{ m}, \quad \beta l = \frac{1}{4} \times 97 = 24.25 \text{ rad} = 309.42^\circ$$

$$Z_{in} = 60 \left[ \frac{j40 + j60 \tan 309.42^\circ}{60 - 40 \tan 309.42^\circ} \right] = -j18.2 \Omega$$

$$V = V_L e^{j\beta l} = (0.575 \angle -250.4^\circ) e^{j309.42^\circ}$$

$$\Rightarrow \boxed{V = 0.575 \angle 59.02^\circ}$$