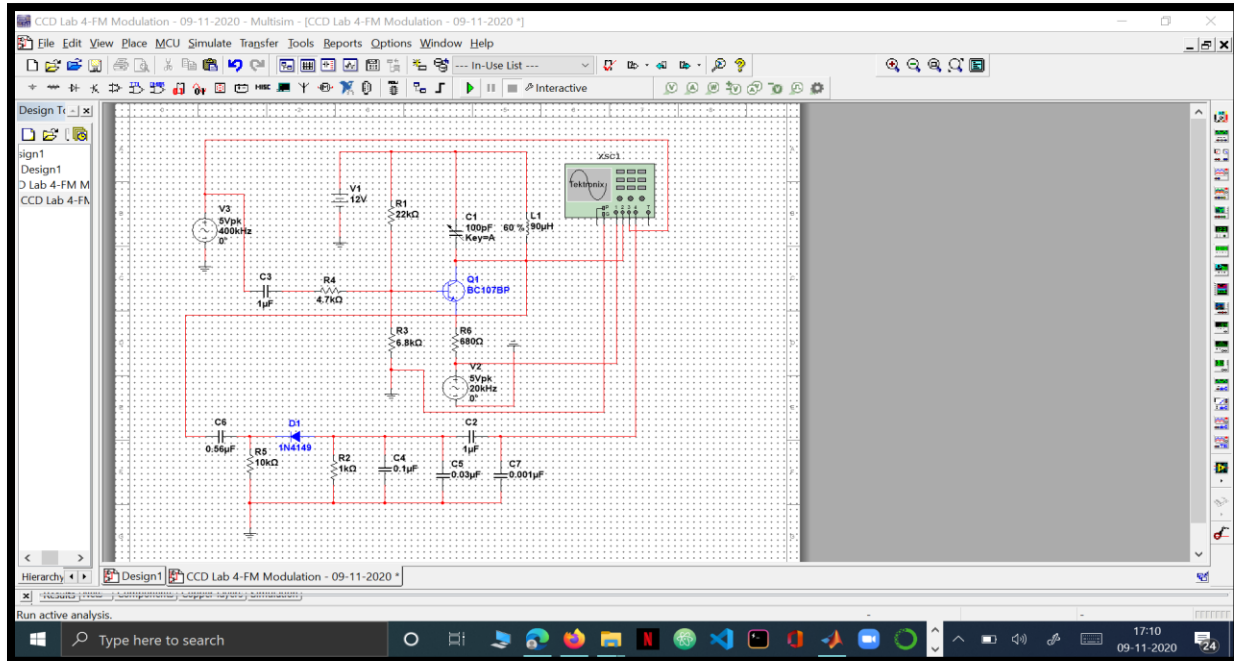


CCD LAB EXPERIMENT: 4

AIM: To find out the output Modulated and Demodulated waveforms using the FM modulation and demodulation techniques using NI Multisim Software.


FM MODULATOR AND DEMODULATOR:

CIRCUIT DIAGRAM:



OUTPUT WAVEFORM ON THE OSCILLOSCOPE:

Carrier and Modulating Signal

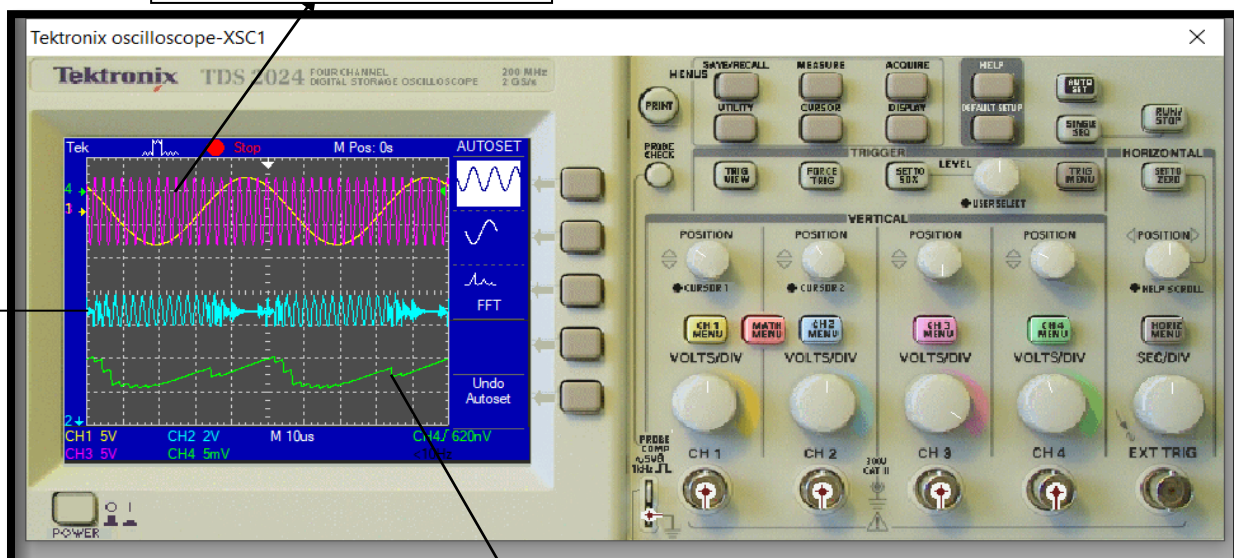

Modulated Signal

Demodulated Signal

Conclusion: Observed the output modulated and demodulated waves using FM Modulation and Demodulation Techniques on a Carrier and a modulating signal and simulated the circuit design by using NI Multisim Software.